



Project Presentation

EEE 206 Sessional

Bangladesh University of Engineering and Technology

29 August 2022




**Bangladesh University of Engineering and Technology
2022**

Overview


- 01** Objectives
- 02** Introduction
- 03** Theoretical
- 04** Equipment
- 05** Procedure

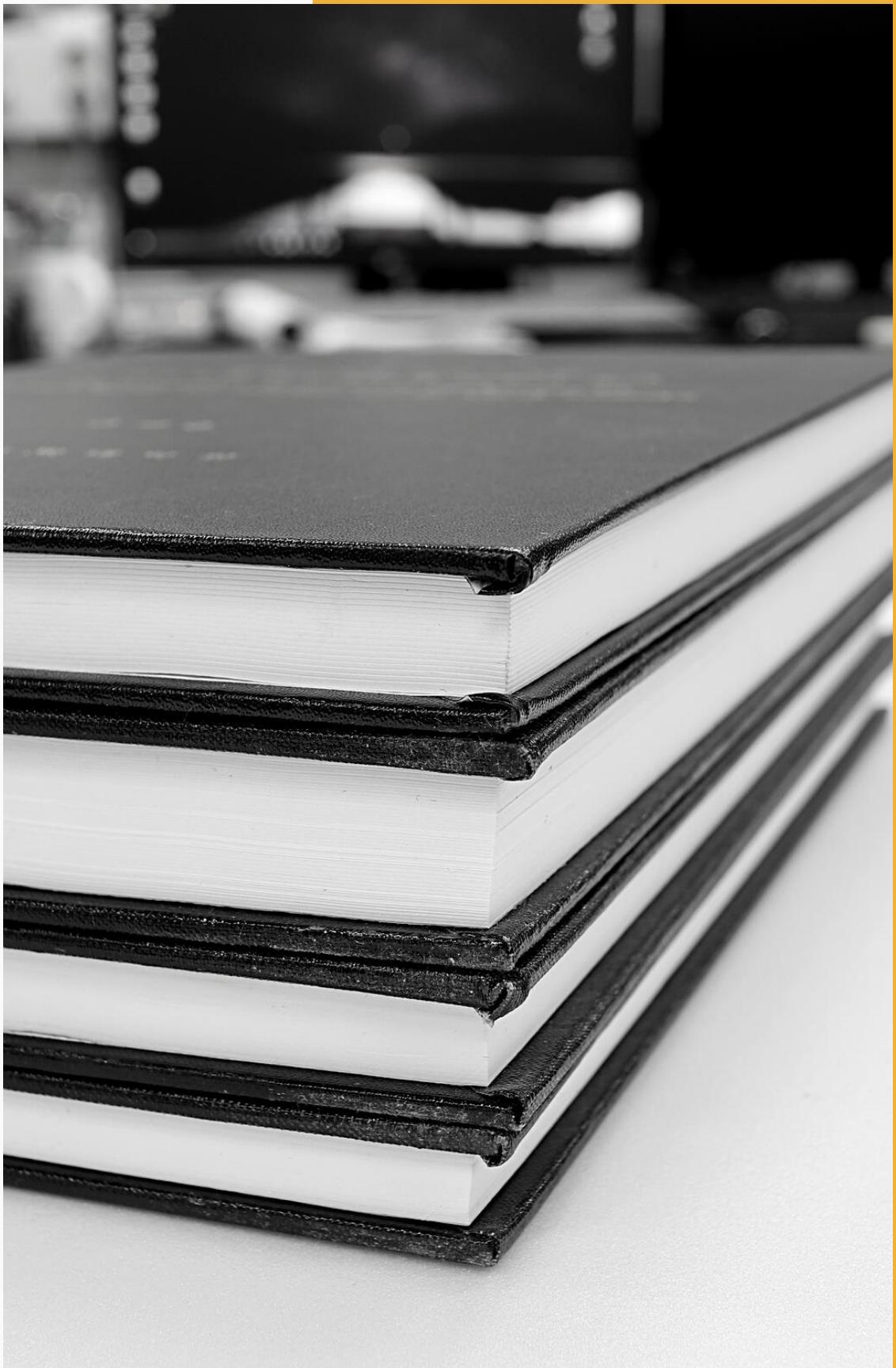- 06** Implementation
- 07** Testing & Results
- 08** Analysis
- 09** Limitation & Application
- 10** Conclusions





Objective

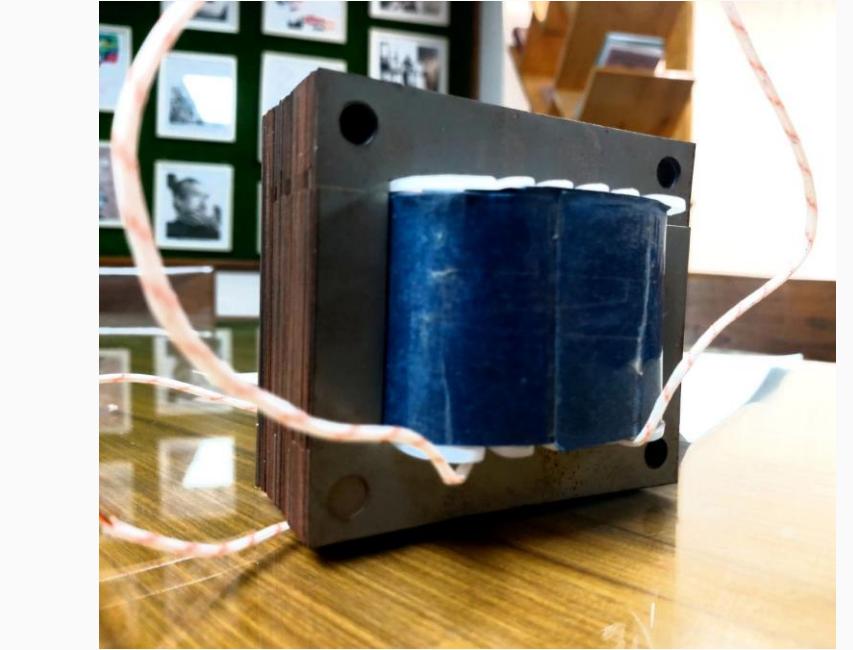

Make Step-Down Transformer of 100VA

Supervisors



Sadman Sakib Ahbab
Lecturer
EEE, BUET



Bijoy Sikder
Lecturer
EEE, BUET



Debashish Roy
Lab Assistant
EEE, BUET



Meet the Team



Eftikhar Sadiq

Md. Liton Ali

Toki Bin Alam

Anindya K
Choudhury


Abid Musfiq

Ahnaf Rasheed

Ramim Hasan

Shawn



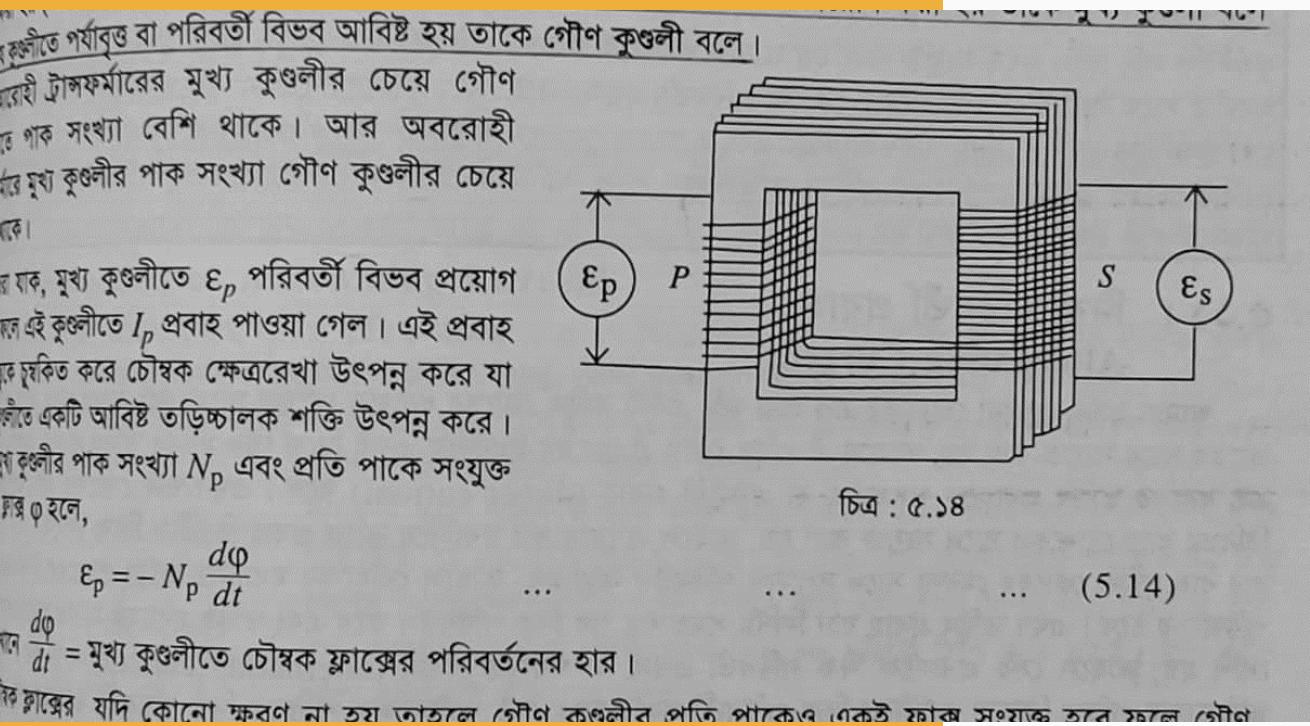

Introduction

CHAPTER 2

TRANSFORMERS



The First Topic of Power- Transformer





The first topic of the first power course-
Transformer

Theoretical

Faraday's Law


Electromagnetic and Mutual Induction

Power Supply Through Transformer

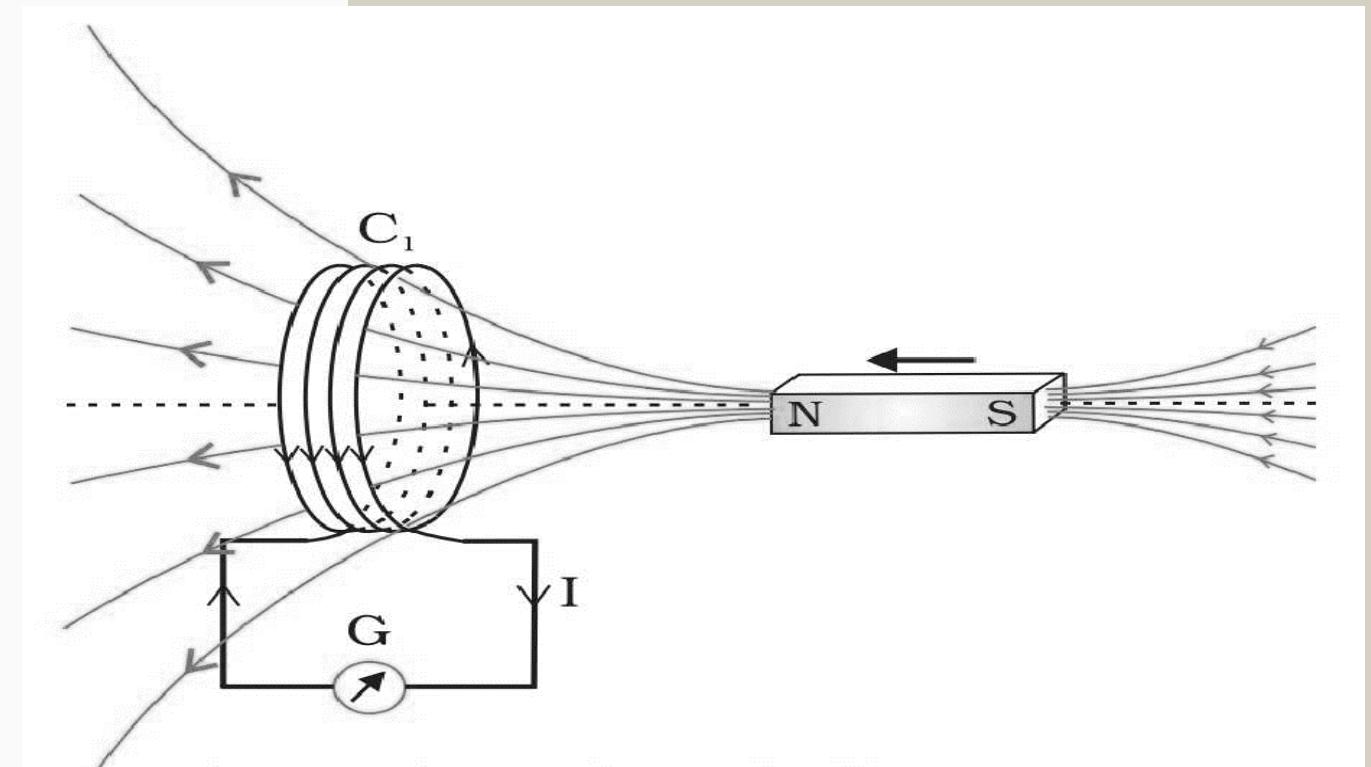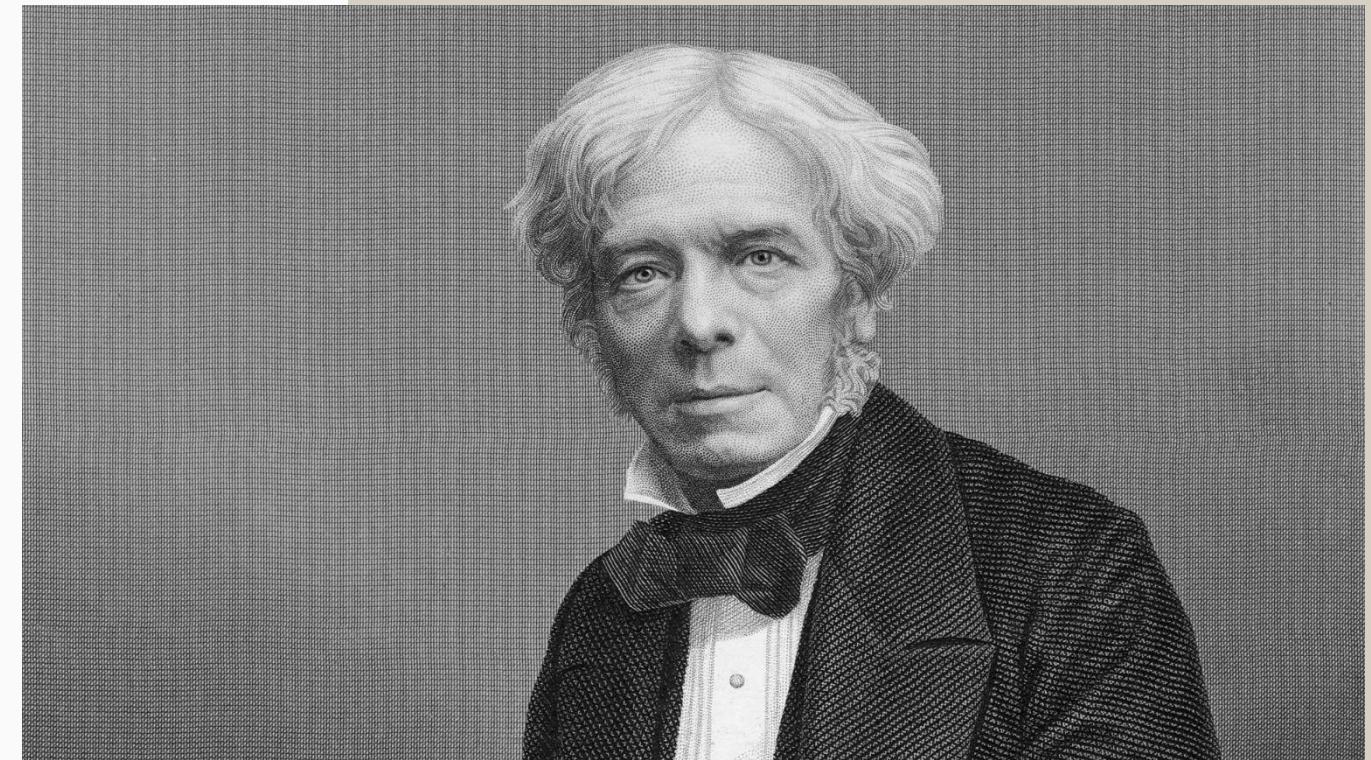


Theoretical

Faraday's Law

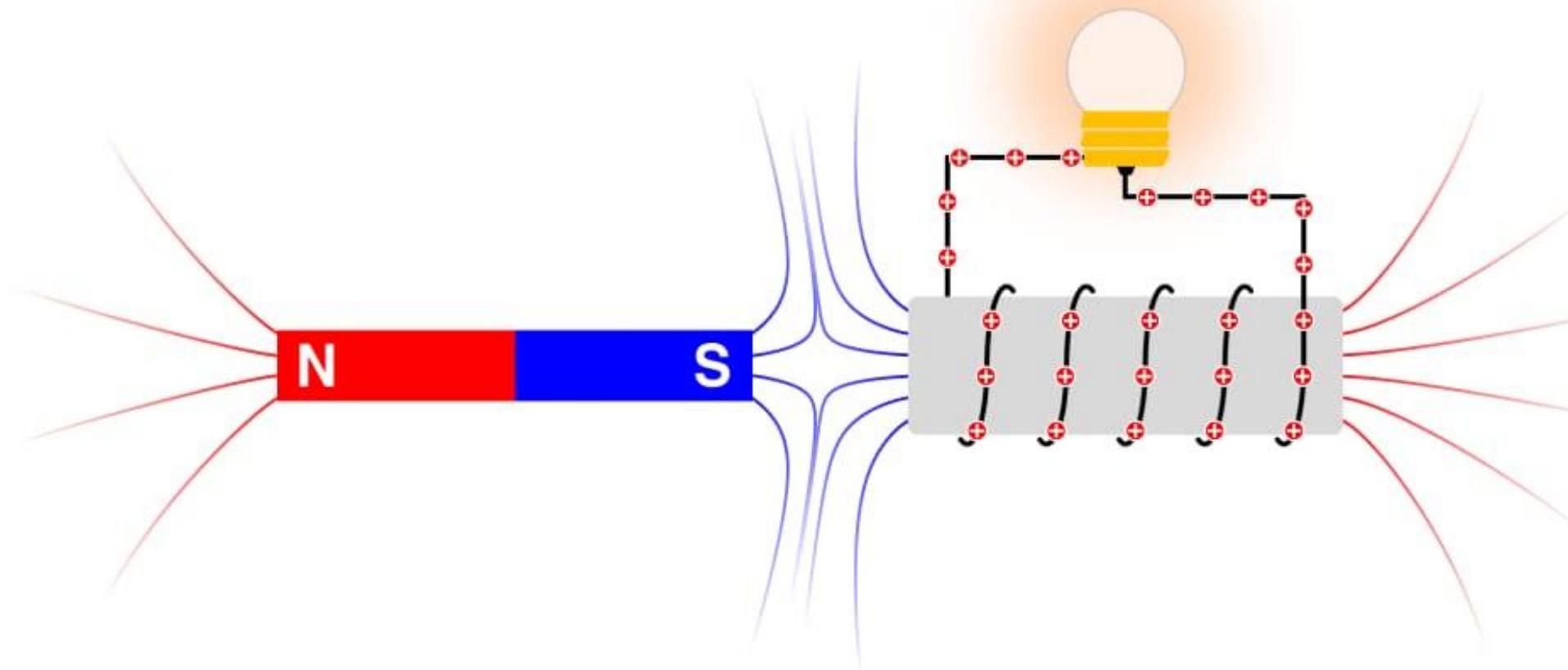


Theoretical


Electromagnetic and Mutual Induction

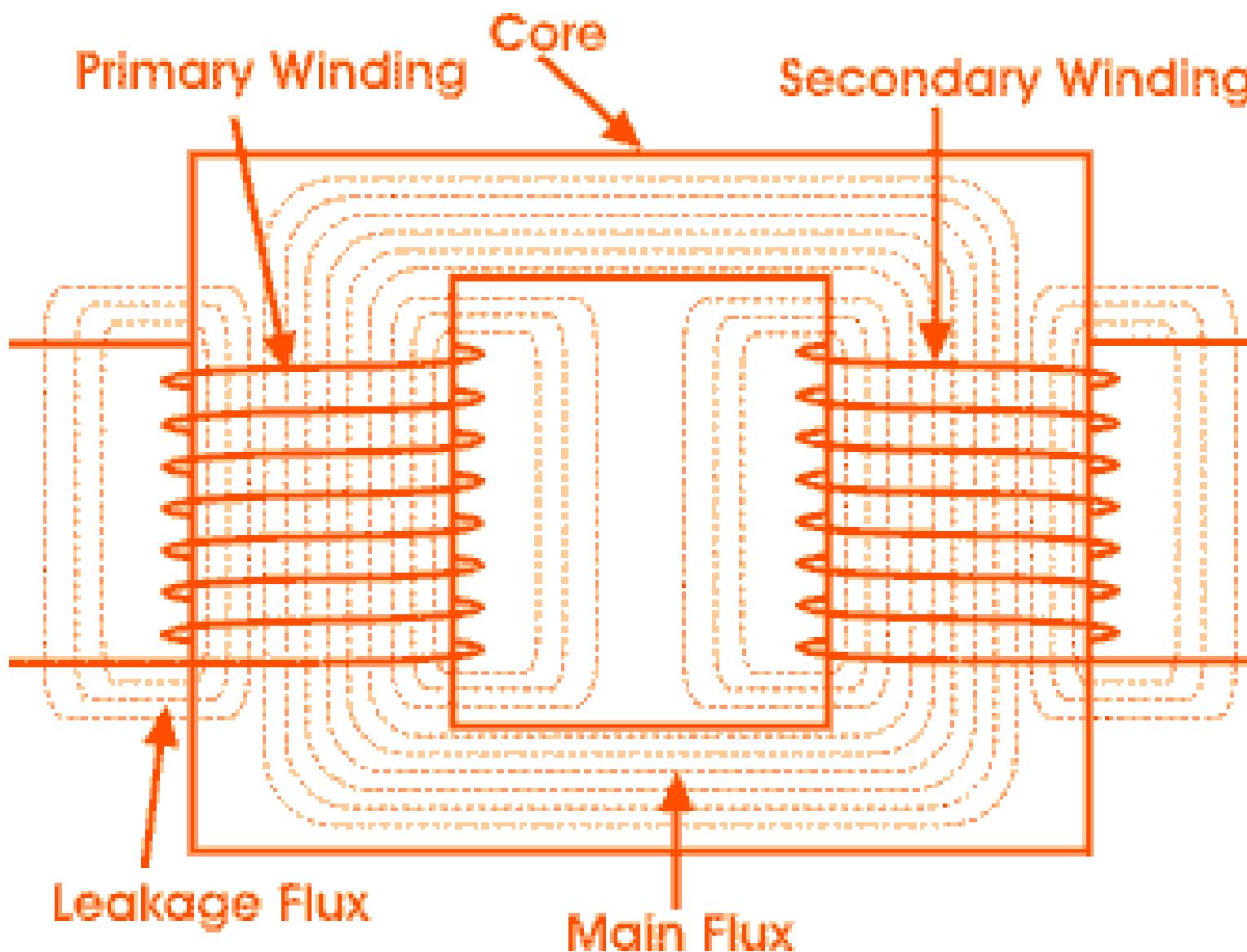

Theoretical

Power Supply Through Transformer

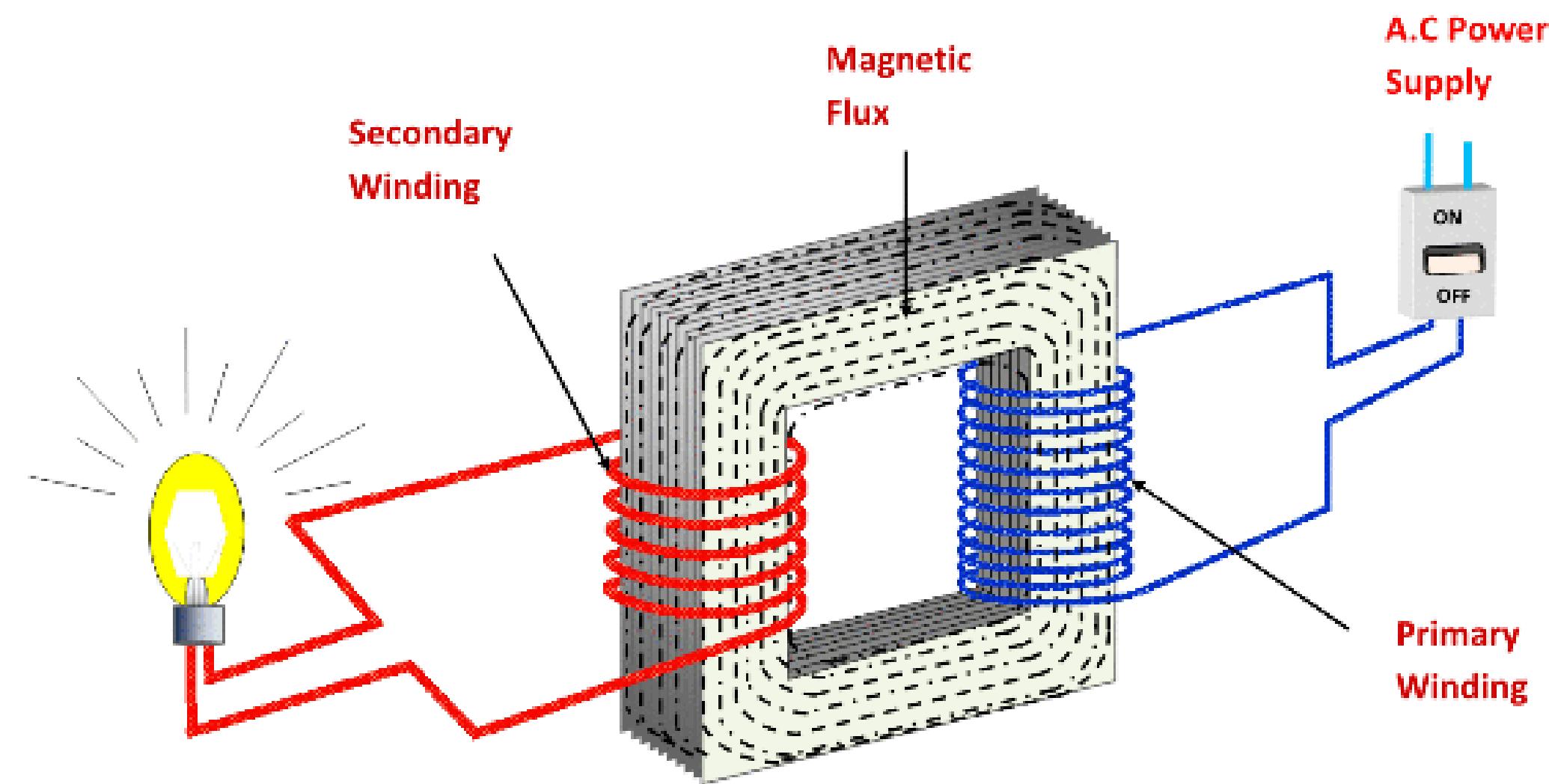

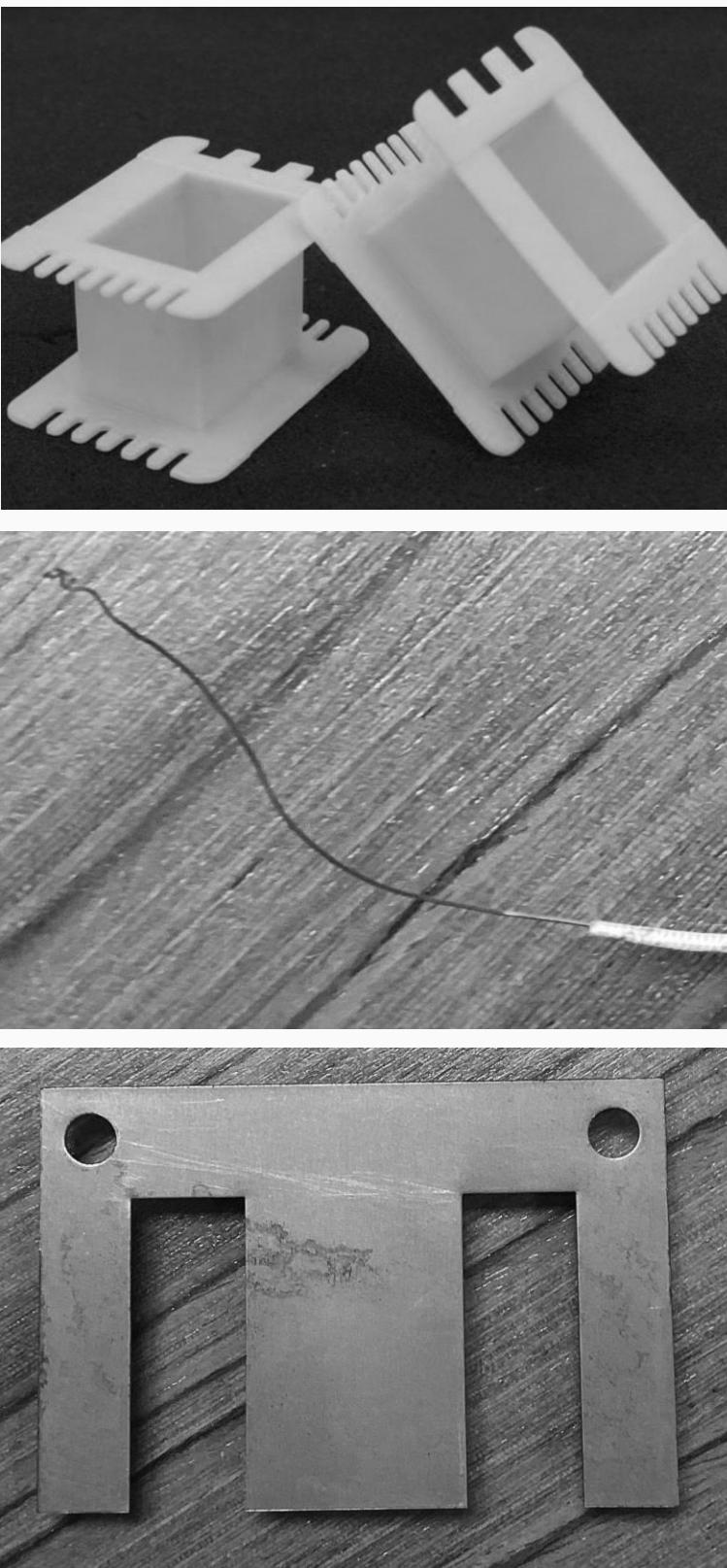

Equipment

1. I Core
2. E Core
3. Wires
4. Bobbin
5. Scotch Tape
6. Lighter
7. Insulation Paper
8. Lab E-Volt Machine for Testing

Procedure




Wiring the Bobbin

- HT side wiring with 960 turns
- Wrapping Insulation Paper
- LT side wiring with 480 turns
- Final wrapping using insulation paper



Assembling the cores


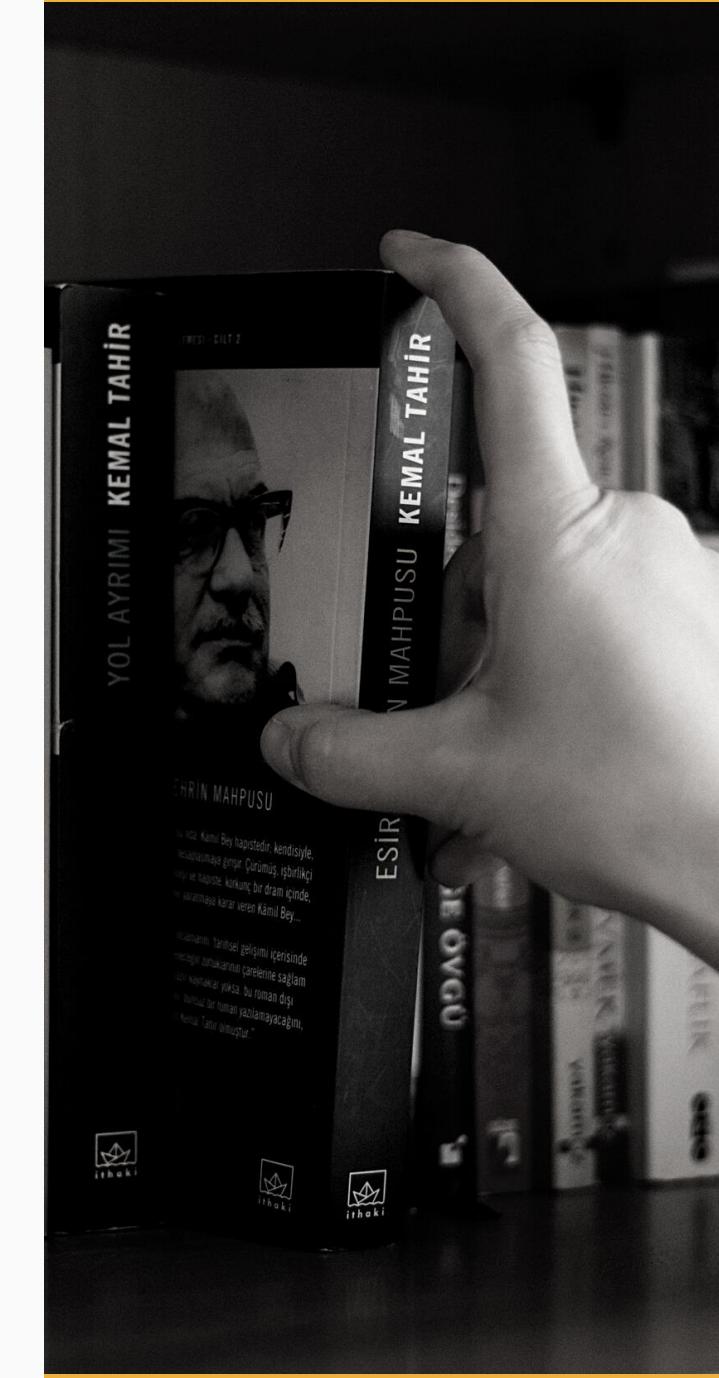
- Inserting E and I shaped cores in the bobbin.



Implementation



Testing

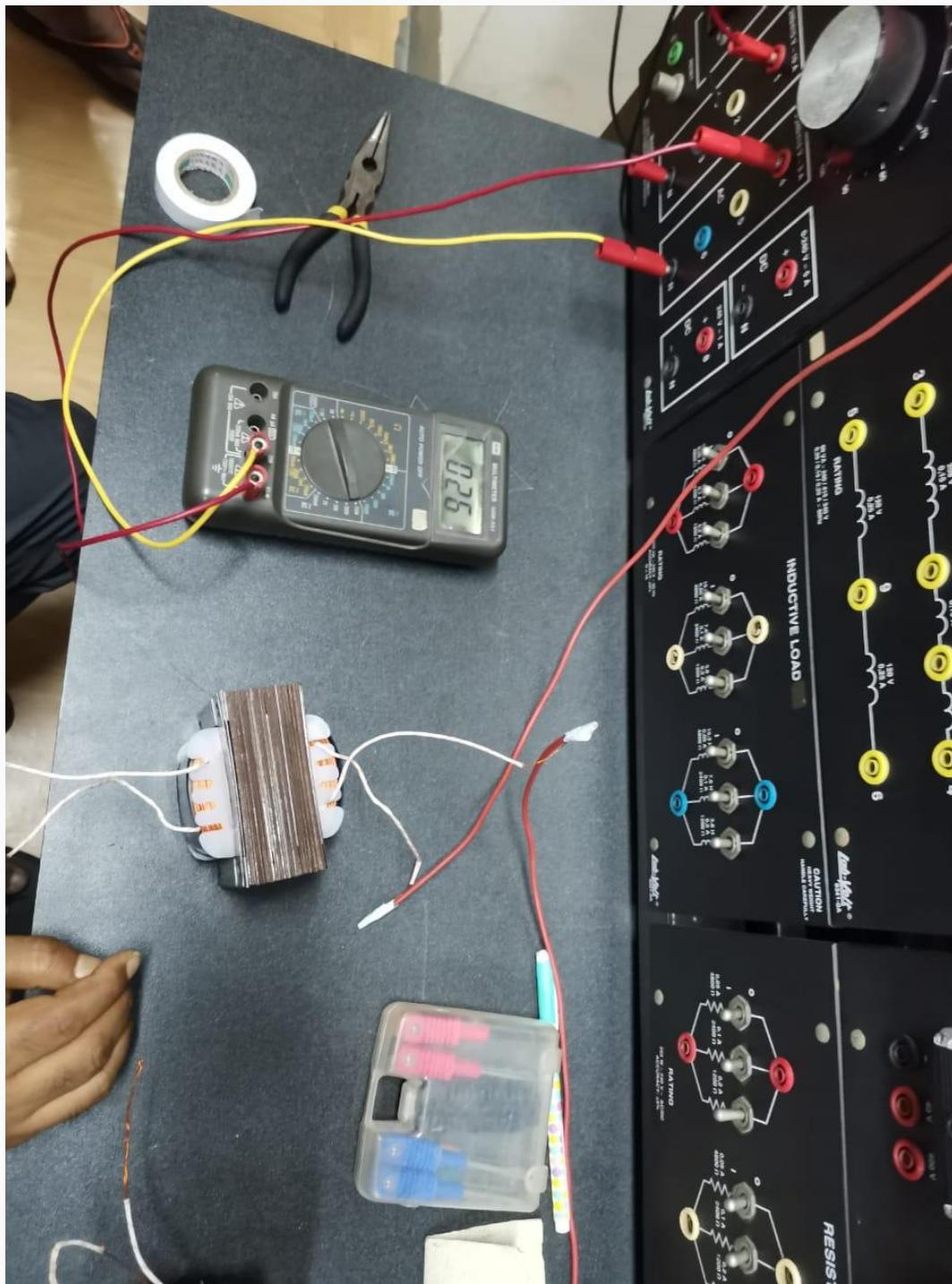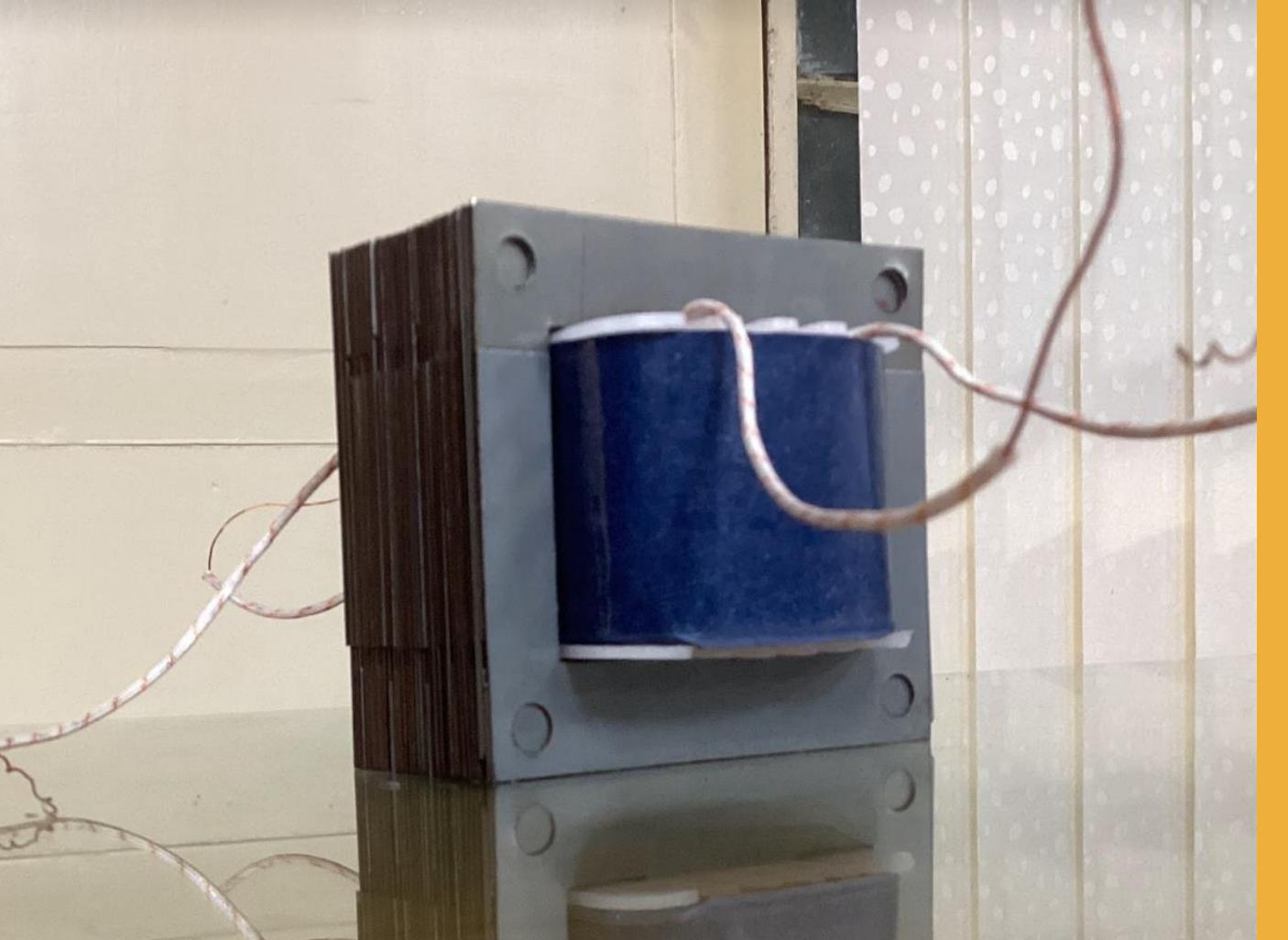

Results

The results of this study can be concluded into the following points:

2022

Both open circuit test and short circuit test was done at HT side of the transformer. We get the following data:

Open Circuit Test		Short Circuit Test	
P_{oc}	5 W	P_{sc}	10 W
V_{oc}	240 V	V_{sc}	26 V
I_{oc}	0.22 A	I_{sc}	0.416 A

Results

The results of this study can be concluded into the following points:

After Applying rated voltage of 240V at primary, at secondary we get

$$V_p = 240V$$

$$V_s = 109.5$$


$$\text{Turns Ratio, } a = \frac{V_p}{V_s} = 2.2$$

Results

The results of this study can be concluded into the following points:

2022

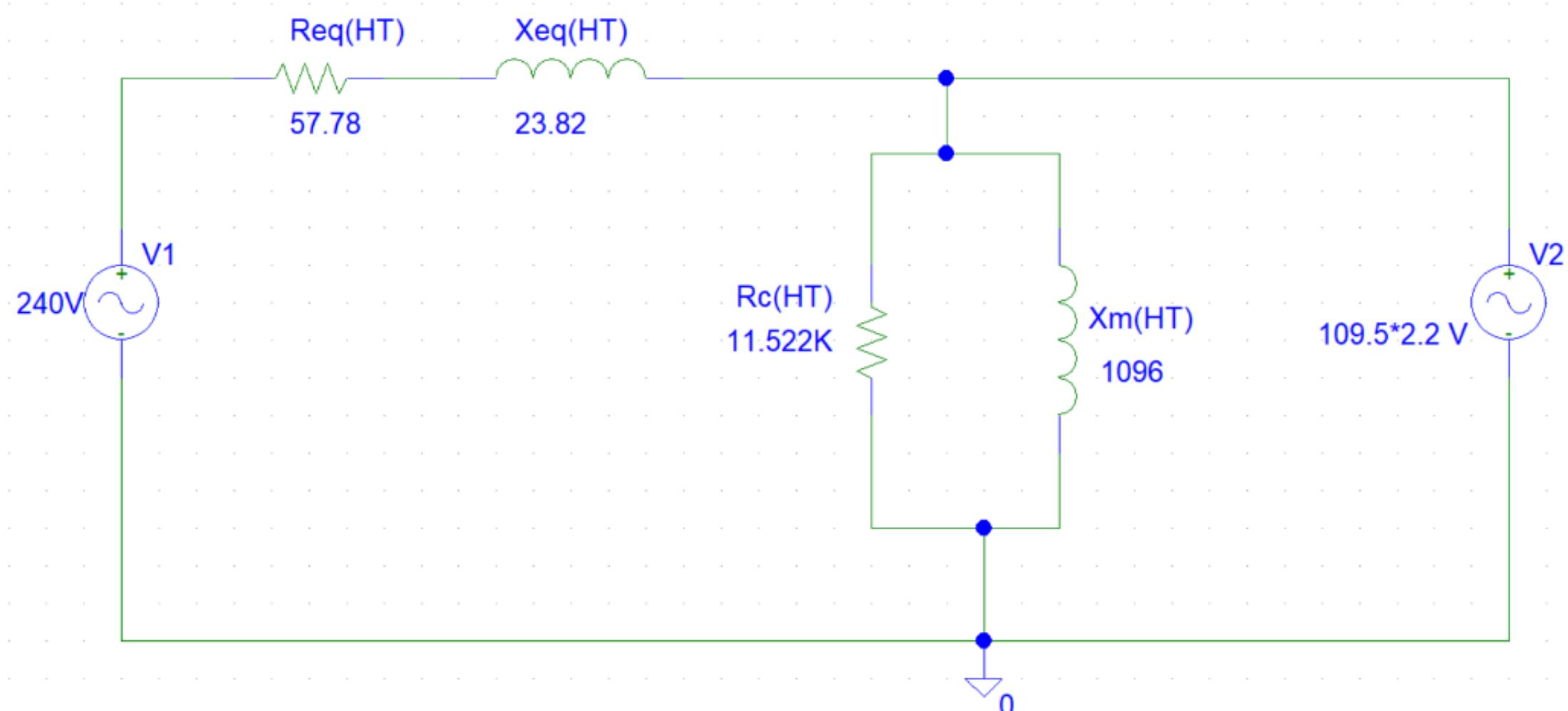The final equivalent circuit of the transformer in terms of HT side/Primary side:



Analysis



- Error in Turns Ratio
- Value of R_c and X_m is quite acceptable.



- The Unavailability of Core and Bobbin of Accurate Size
- Air Gap in the Core
- Inexperience in Winding





Limitation



- Limited Time Period
- Inaccessibility to Marketplaces
- Scheduled Load-shedding Period
- Unavailability of Quality Raw Materials
- Unavailability of Auto Winding Machine

Applications

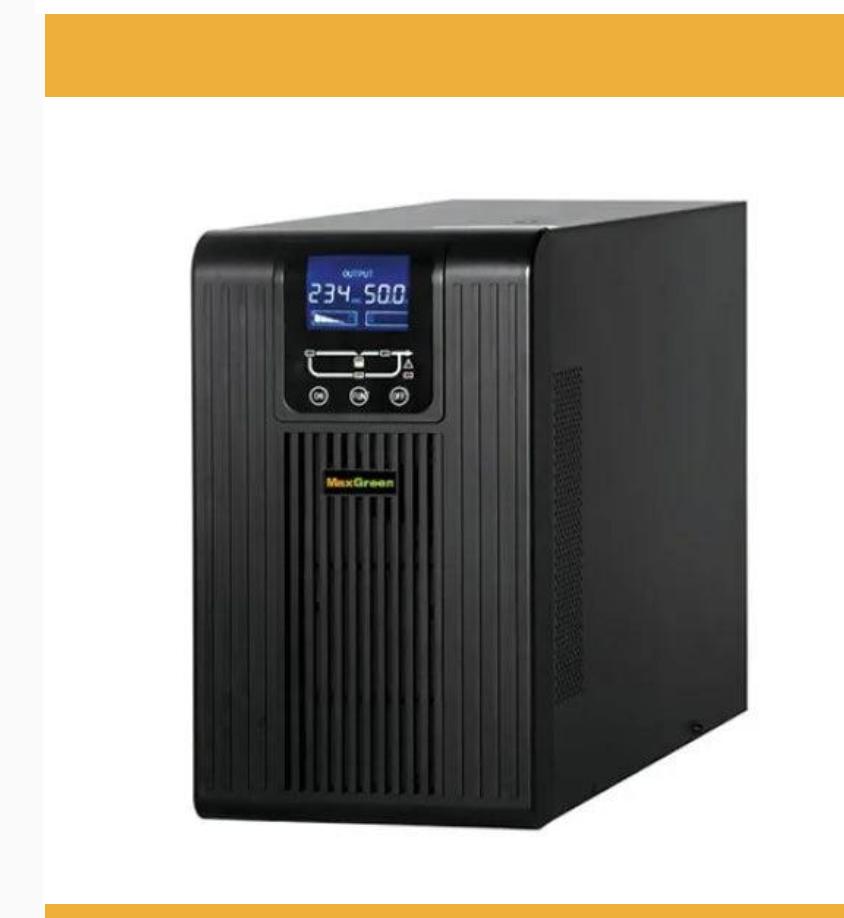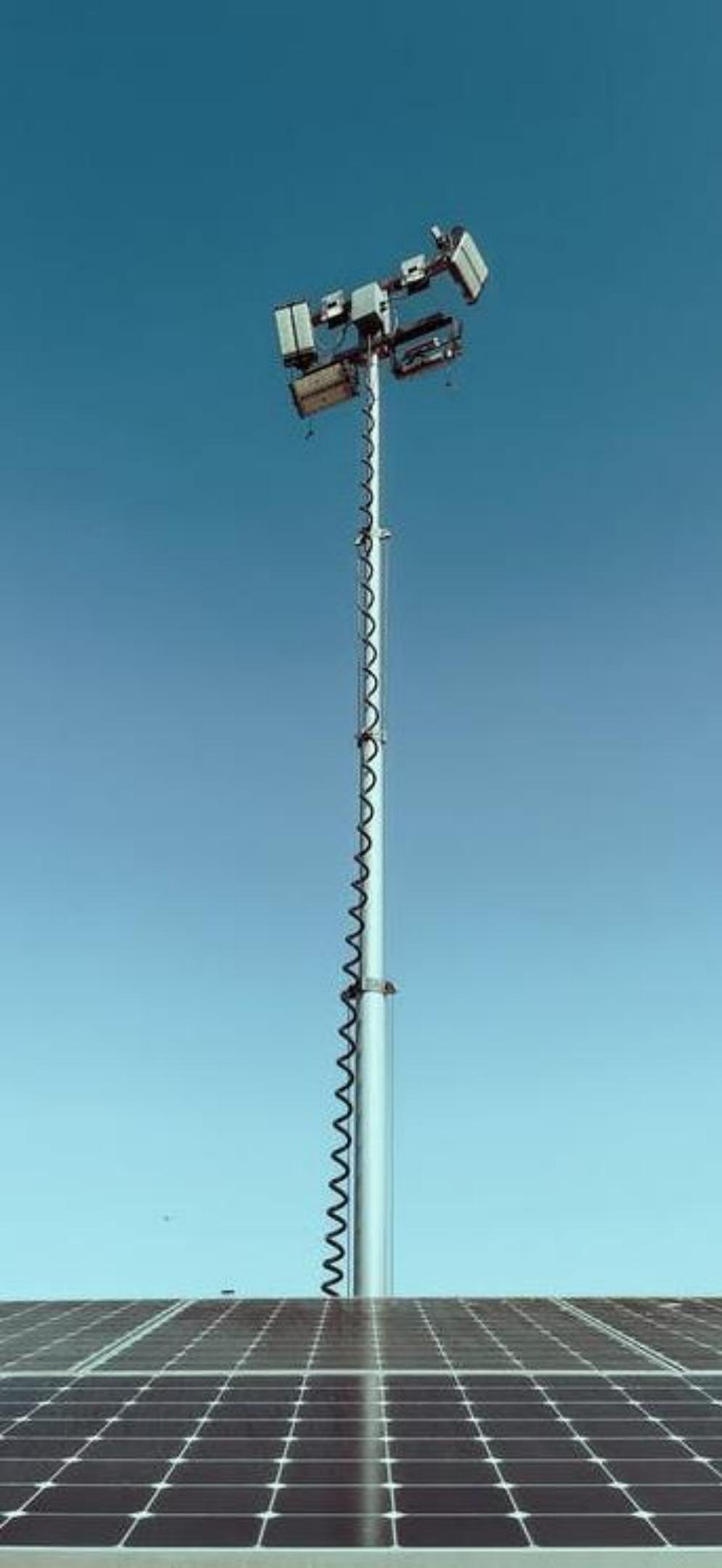- Portable Voltage converter
 - UPS
 - Solar Panel



Conclusion

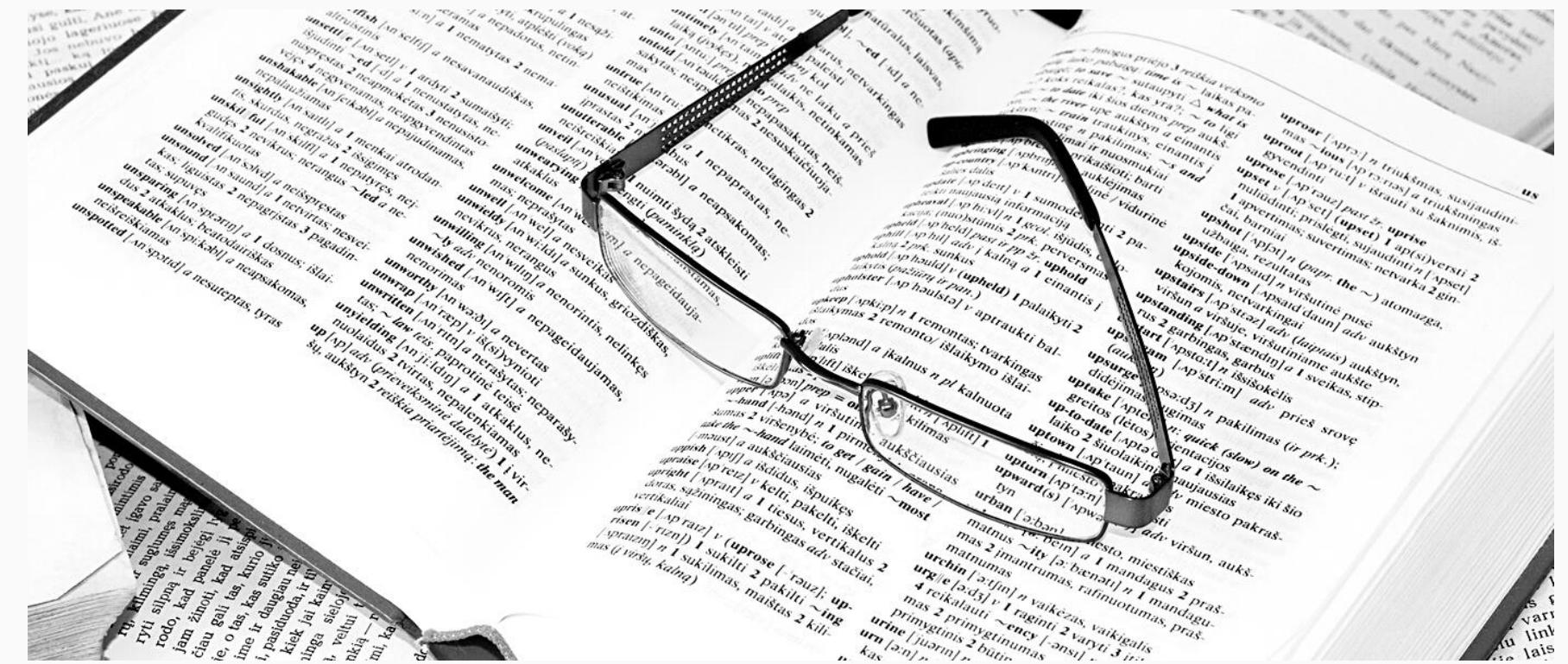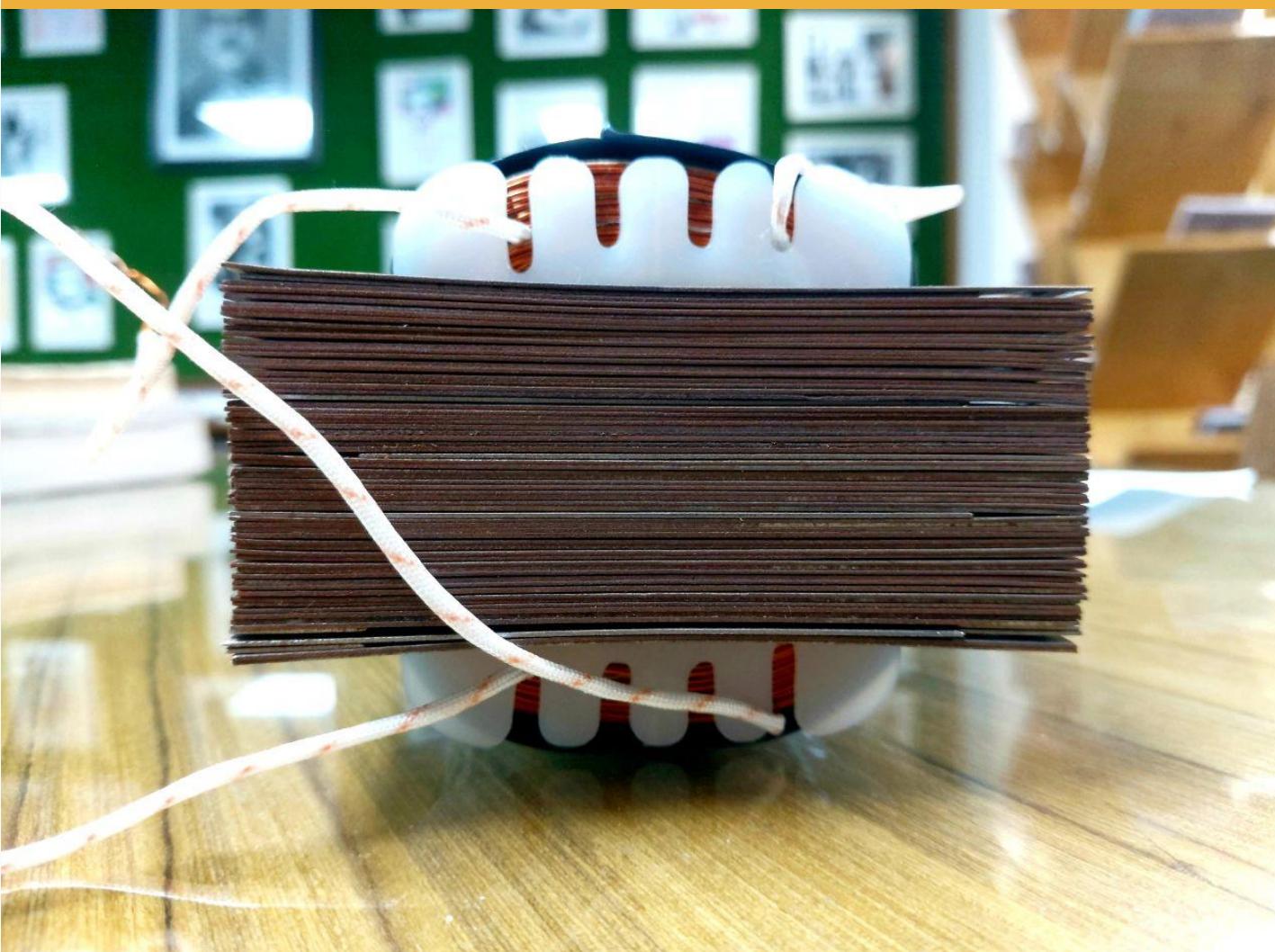

The Project is successful in imparting the key structural concepts of transformer.

Thank You

Q & A Session

Results Appendix

The results of this study can be concluded into the following points:

- From open circuit test,

$$\text{Power factor angle, } \theta = \cos^{-1} \frac{P_{oc}}{V_{oc} \times I_{oc}} = 84.567 \text{ degree}$$

$$\text{Admittance, } Y_E = \frac{I_{oc}}{V_{oc}} \angle -\theta = \frac{1}{R_C} - j \frac{1}{X_M} = 8.679 \times 10^{-5} - j(9.1255 \times 10^{-4})$$

$$R_C = 11.522 \text{ k}\Omega$$

$$X_M = 1096 \Omega$$

- From short circuit test,

$$\text{Power factor angle, } \theta = \cos^{-1} \frac{P_{sc}}{V_{sc} \times I_{sc}} = 22.398 \text{ degree}$$

$$\text{Impedance, } Z_{SE} = \frac{V_{sc}}{I_{sc}} \angle \theta = R_{eq} - j X_{eq} = 57.78 + 23.82j$$

$$R_{eq} = 57.78 \Omega$$

$$X_{eq} = 23.82 \Omega$$

Pre-Calculation Appendix

The results of this study can be concluded into the following points:

Rating: 240V/120V Step down transformer

Apparent Power: 100 VA

Current Rating:

Primary:

$$V_P = 240 \text{ V}$$

$$I_{P, \max} = \frac{S}{V} = \frac{100}{240} \text{ A} = 0.41667 \text{ A}$$

Secondary:

$$V_S = 120 \text{ V}$$

$$I_{S, \max} = \frac{S}{V} = \frac{100}{120} \text{ A} = 0.833 \text{ A}$$

Pre-Calculation Appendix

The results of this study can be concluded into the following points:

2022

SWG of Wire selection:

	SWG number	Current Capacity, A	
Primary	SWG 27	0.359	0.538
Secondary	SWG 23	0.768	1.15

Finding Bobbin Size:

$$\text{Bobbin Area} = \frac{\sqrt{VA}}{6.32} = \frac{\sqrt{100}}{6.32} = 1.58 \text{ inch}^2$$

Pre-Calculation Appendix

The results of this study can be concluded into the following points:

2022

Finding Turns Ratio:

$$\text{Turns per volt, TPV} = \frac{1}{4.44fBA}$$

Where,

Frequency, $f = 50 \text{ Hz}$

Magnetic Flux density, $B = 1.2 \text{ T}$

Bobbin Area, $A = 11.52 \times 10^{-4} \text{ m}^2$

$$\text{TPV} = \frac{1}{4.44 \times 50 \times 1.2 \times 11.52 \times 10^{-4}} = 3.23 \approx 4$$

Primary Winding Turns = $240 * \text{TPV} = 960$

Secondary Winding Turns = $120 * \text{TPV} = 480$

Total wire Required:

Bobbin Perimeter = $2(L+W) = 2(1.5+1.25) \text{ inch} = 5.5 \text{ inch} = 0.1397 \text{ m}$

Total wire for primary = $960 * 0.1397 \text{ m} = 134.112 \text{ m}$

Total wire for secondary = $480 * 0.1397 \text{ m} = 67.056 \text{ m}$